

CSE 250 : Circuits and Electronics

Experiment 02

Introduction to series and parallel circuits

Name : Anika Islam

ID: 21101298

Section: 06

Group: 01

Semester: Fall '22

Date of performance: 16/10/2022



Date of submission: 23/10/2022

REPORT

Result Table for circuit 1

R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	R_4 (k Ω)		R_{eq} (k Ω)	I_1 (mA)	I_2 (mA)	$V_{3,4}$ (V)	I (mA)	$I = I_1 + I_2$ (mA)
0.98	0.98	0.98	0.98	Experimental	2.46	1.2	1.19	4.7	2.398	2.39
				Theoretical	2.46	1.22	1.22	4.8	2.449	2.44

(Circuit diagram for circuit 1)

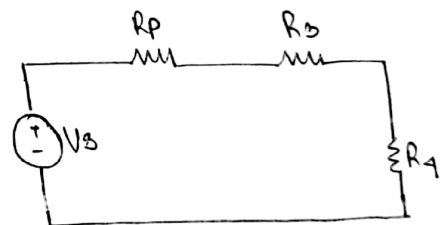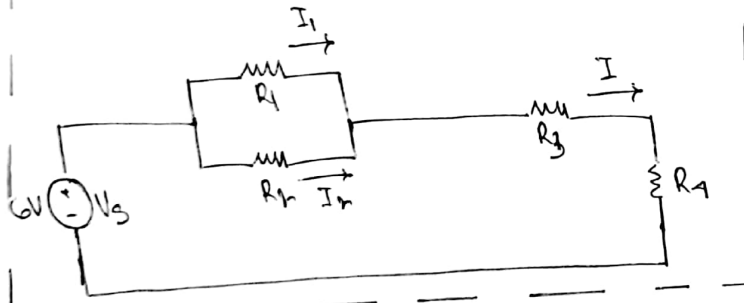

CALCULATIONS:-

$$R_p = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{0.98} + \frac{1}{0.98} \right)^{-1} = 0.49 \text{ k}\Omega$$

$$R_{eq} = R_p + R_3 + R_4 = 0.49 + 0.98 + 0.98 = 2.45 \text{ k}\Omega$$

$$I = \frac{V_3}{R_{eq}} \Rightarrow I = \frac{6}{2.45} = 2.449 \text{ mA}$$

$$I_1 = \frac{R_2}{R_1 + R_2} \times I \Rightarrow \frac{0.98}{0.98 + 0.98} \times 2.449 = 1.22 \text{ mA}$$




$$I_2 = \frac{R_1}{R_1 + R_2} \times I \Rightarrow \frac{0.98}{0.98 + 0.98} \times 2.449 = 1.22 \text{ mA}$$

$$V_{3,4} = \frac{R_3 + R_4}{R_{eq}} \times V \Rightarrow \frac{0.98 + 0.98}{2.45} \times 6 = 4.8 \text{ V}$$



Result Table for Circuit 2

R (k Ω)	R ₁ (k Ω)	R ₂ (k Ω)	R ₃ (k Ω)	R ₄ (k Ω)	R ₅ (k Ω)	Observation	I ₁ (mA)	I ₂ (mA)	I ₃ (mA)	I ₄ (mA)	I _{1,2} = I ₃ + I ₄ (mA)	I ₀ (mA)	I = I ₁ + I ₂ (mA)	R _{eq} (k Ω)
0.98	0.98	0.98	0.98	0.98	0.98	Experimental	1.60 1.38	2.31	0.92	0.45	1.37	3.68	3.69	1.60
						Theoretical	1.88 1.267	1.88 2.50	0.94 0.847	0.94 0.422	1.88 1.27	3.77	3.77 3.77	1.59

Calculations:-

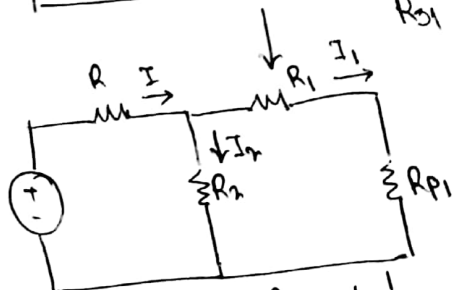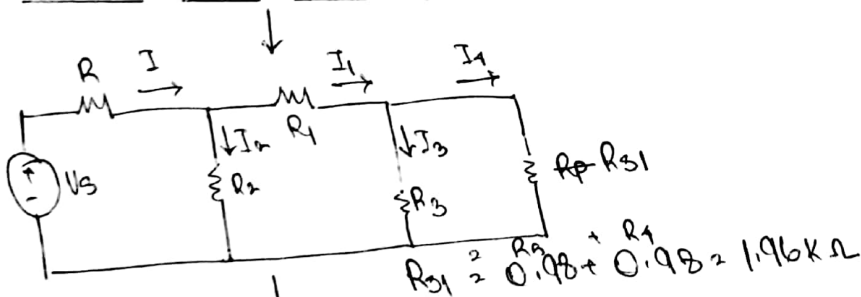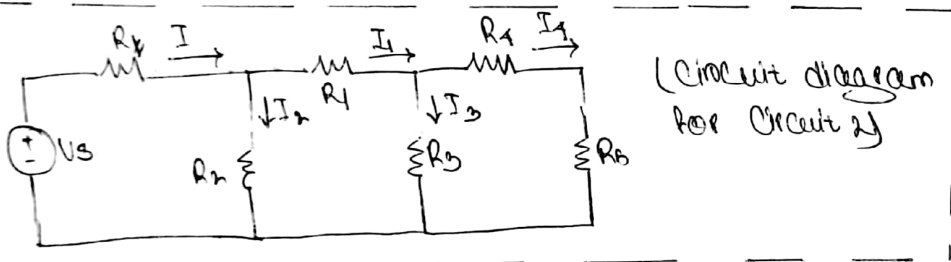
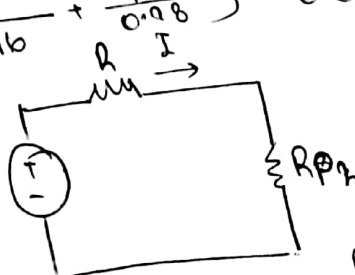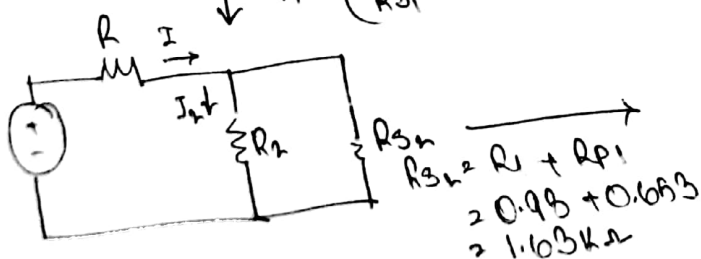
$$R_{p1} = \left(\frac{1}{R_{31}} + \frac{1}{R_1} \right)^{-1} = \left(\frac{1}{1.96} + \frac{1}{0.98} \right)^{-1} = 0.653 \text{ k}\Omega$$



$$R_{p2} = \left(\frac{1}{R_{31}} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{1.96} + \frac{1}{0.98} \right)^{-1} = 0.6125 \text{ k}\Omega$$

$$R_{eq} = R_{p2} + R = 0.6125 + 0.98 = 1.59 \text{ k}\Omega$$

$$I = \frac{V_s}{R_{eq}} \Rightarrow I = \frac{6}{1.59} = 3.77 \text{ mA}$$

$$I_{01} = \left(\frac{\frac{1}{R_2 + R_4} + \frac{1}{R_3}}{\frac{1}{R_2 + R_4} + \frac{1}{R_3} + \frac{1}{R_5}} \right) \times I = \frac{\left(\frac{1}{0.98} + \frac{1}{0.98} + \frac{1}{0.98} \right)}{0.98} \times 3.77 = 1.88 \text{ mA} \quad 1.27 \text{ mA}$$

$$I_2 = I - I_1 \Rightarrow I_2 = 3.77 - 1.27 = 1.88 \text{ mA} \quad 2.60 \text{ mA}$$

$$I_4 = \left(\frac{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5}} \right) \times I = \frac{\left(\frac{1}{0.98} + \frac{1}{0.98} + \frac{1}{0.98} \right)}{0.98} \times \frac{1.88}{1.267} = 0.94 \text{ mA} \quad 0.423 \text{ mA}$$

$$I_3 = I_4 - I_1 = 1.88 - 0.94 = 0.94 \text{ mA}$$

$$= 1.26 - 0.417 = 0.423$$

$$= 1.27 - 0.423 = 0.847 \text{ mA}$$


Comment on the obtained results and discrepancies (if any)

For circuit 1: The difference between the experimentally obtained results and theoretically obtained results are very close enough. Thus, showing almost no significant change in values between the experimental values and theoretical values.


For circuit 2: There is ^{almost no} significant difference between the experimentally obtained values and theoretically obtained values of I_1, I_2, I_3, I_4 and almost no difference ^{for} between the values of I_5, R_{eq} and I . The ^{slight} significant differences may have occurred due to ~~get~~ fluctuations of readings on the multimeter while taking the readings. Also, the DC power supply was supposed to provide 6V voltage. But, there was a fluctuations in the power supply as well. ~~There may be an~~

QUESTION

(1)


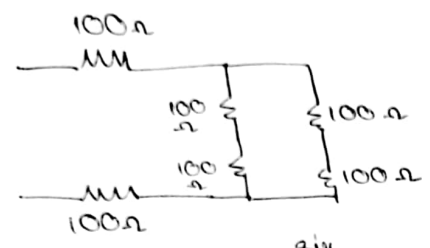


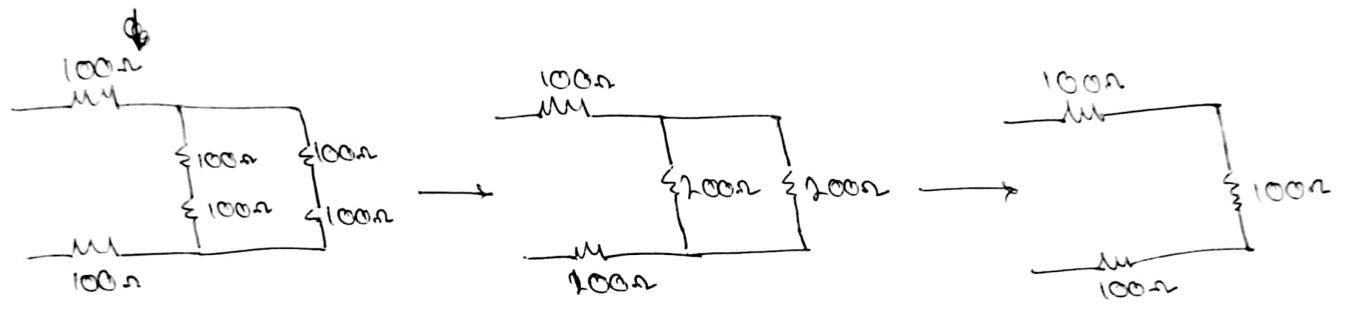(Arrangement of 3 \times 100Ω resistors to provide 300Ω resistance)




~~Req =~~ $Req = 100 + 100 + 100 = 300\Omega$

(2)

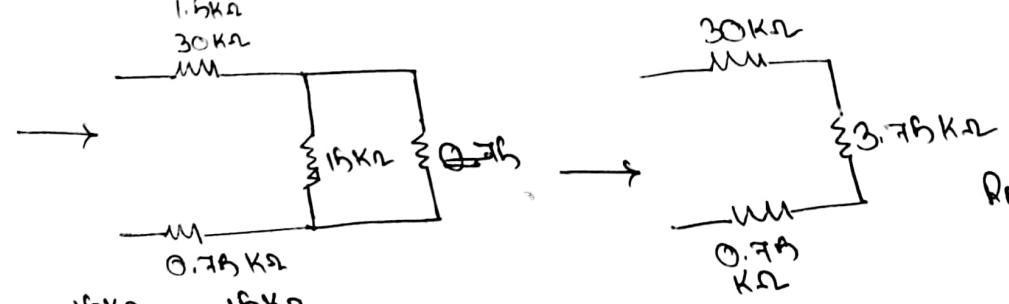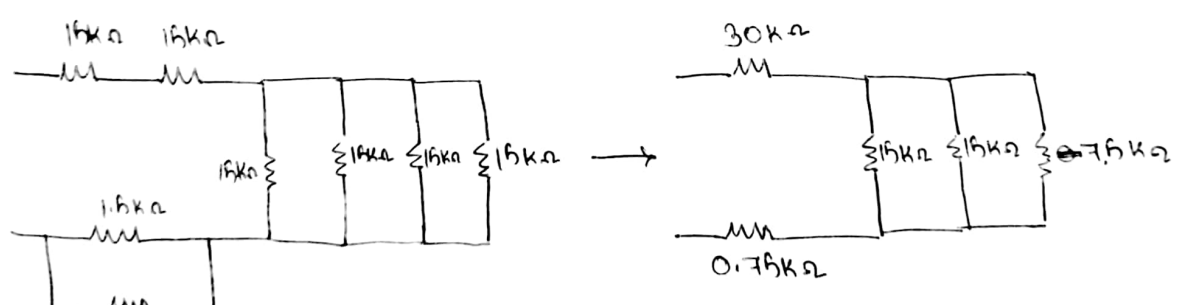

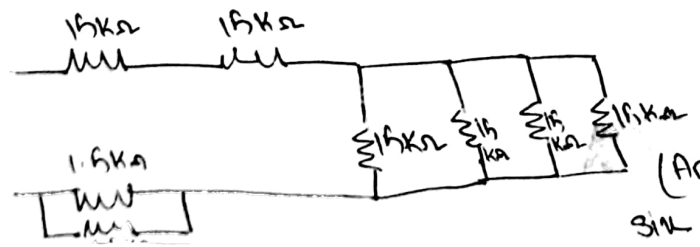$Req = 30 + 0.75 + 0.375 = 31.125k\Omega$



(Arrangement of two 15kΩ & six 15kΩ resistors to provide 31.125kΩ resistance)

Discussion

Both the circuits (Circuit 1 and Circuit 2) were connected on the trainer board ~~using~~ ~~DE-PO~~ using the circuit diagram ~~from the~~ without thinking about any parallel or series ~~or~~ connection to avoid confusion during the process.

Voltage was measured for all the voltages asked in the data table; ~~using~~ by connecting multimeter across the nodes of the resistors and setting the multimeter ~~at~~ volt to measure voltage using the knob. Also, resistors were connected on the trainer board before building up the circuit and using the multimeter across both ends, resistance is measured.

Since we had the necessary voltages and resistances, we calculated current using Ohm's law. ~~Using multimeter~~ To measure current, the multimeter needs to be connected in series with the resistors; leading to opening up the circuit. Thus, gives inaccurate current values. So, ~~it is not there~~ is no need to measure current directly.

BRAC UNIVERSITY
DEPT. OF COMPUTER SCIENCE AND ENGINEERING
COURSE NO.: CSE250
Circuits and Electronics Laboratory

Experiment No. 2

Name of the Experiment: Introduction to series and parallel circuits.

Group No.: 01

Signature of lab faculty: *Purlyan*

Date: 16-10-2027

Table 1: For circuit 1

Observation	Experimental	Theoretical
$R_{eq}(K\Omega)$	1.7042.46	2.45

Table 2: For circuit 1

R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	R_4 (k Ω)	Observation	$I_1 = V_{R1}/R_1$ (mA)	$I_2 = V_{R2}/R_2$ (mA)	$V_{3,4}$ (V)	$I = \frac{V_{3,4}}{R_3 + R_4}$ (mA)	$I = I_1 + I_2$ (mA)
0.98 ✓	0.98	0.98	0.98	Experimental	$I_1 = \frac{1.176}{0.98}$ $= 1.2$	$I_2 = \frac{1.17}{0.98}$ $= 1.19$	4.7	$I = \frac{4.7}{0.98 + 0.98}$ $= 2.398$	$I = 1.2 + 1.19$ $= 2.39$
				Theoretical	$I_1 = \frac{0.98}{2.45} \times 6$ $I_1 = 1.2$	$I_2 = 1.2$	4.8	2.449	2.4

Table 3: For circuit 2

Observation	Experimental	Theoretical
$R_{eq}(K\Omega)$	1.60	1.599

Table 4: For circuit 2

R (k Ω)	R ₁ (k Ω)	R ₂ (k Ω)	R ₃ (k Ω)	R ₄ (k Ω)	R ₅ (k Ω)	Observation	$I_1 = \frac{V_{R1}}{R_1}$ (mA)	$I_2 = \frac{V_{R2}}{R_2}$ (mA)	$I_3 = \frac{V_{R3}}{R_3}$ (mA)	$I_4 = \frac{V_{R4}}{R_4}$ (mA)	$I_1 + I_4$ (mA)	$I = \frac{V_R}{R}$ (mA)	$I = I_1 + I_2$ (mA)
0.98	0.98	0.98	0.98	0.98	0.98	Experimental	$\frac{1.35}{0.98} = 1.38$	$\frac{2.26}{0.98} = 2.31$	$\frac{0.9}{0.98} = 0.92$	$\frac{0.44}{0.98} = 0.45$	$0.92 + 0.45 = 1.37$	$\frac{3.61}{0.98} = 3.68$	$1.38 + 2.31 = 3.69$
						Theoretical	$\frac{1.38}{1.27}$	$\frac{1.38}{2.50}$	$\frac{0.94}{0.847}$	$\frac{0.94}{0.823}$	$\frac{0.94}{1.27}$	$\frac{0.9}{3.74}$	$\frac{3.51}{3.51}$

Table 5: For lab task

R ₁ (k Ω)	R ₂ (k Ω)	R ₃ (k Ω)	R ₄ (k Ω)	Observation	$I_1 = \frac{V_{R1}}{R_1}$ (mA)	$I_2 = \frac{V_{R2}}{R_2}$ (mA)	$I_1 + I_2$ (mA)	$I_3 = \frac{V_{R3}}{R_3}$ (mA)	$I_4 = \frac{V_{R4}}{R_4}$ (mA)
				Experimental					
				Theoretical					